

## FSM Design

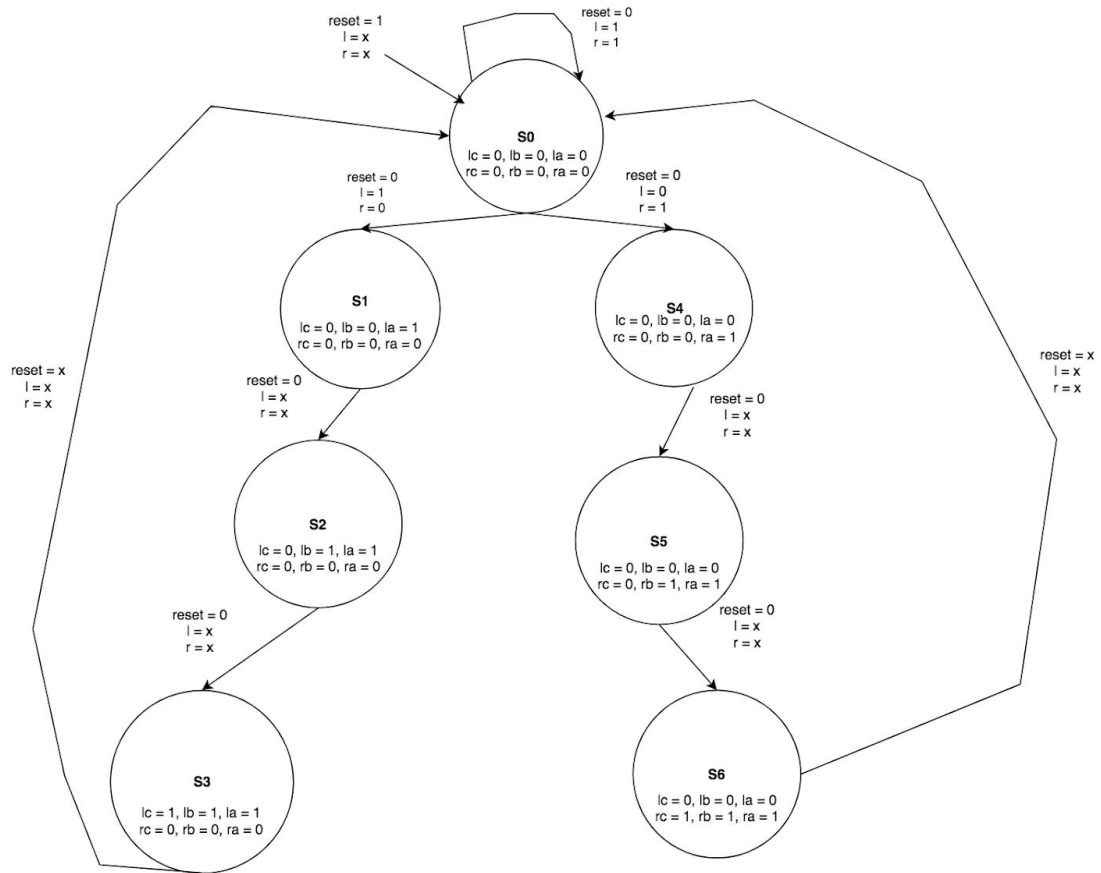


Figure 1: State Diagram

STATE TRANSITION TABLE										
INPUTS			STATES		OUTPUTS					
reset	l	r	PRESENT	NEXT	lc	lb	la	rc	rb	ra
1	x	x	X	S <sub>0</sub>	0	0	0	0	0	0
0	1	0	S <sub>0</sub>	S <sub>1</sub>	0	0	0	0	0	0
0	0	1	S <sub>0</sub>	S <sub>4</sub>	0	0	0	0	0	0
0	1	1	S <sub>0</sub>	S <sub>0</sub>	0	0	0	0	0	0
0	x	x	S <sub>1</sub>	S <sub>2</sub>	0	0	1	0	0	0
0	x	x	S <sub>2</sub>	S <sub>3</sub>	0	1	1	0	0	0
x	x	x	S <sub>3</sub>	S <sub>0</sub>	1	1	1	0	0	1
0	x	x	S <sub>4</sub>	S <sub>5</sub>	0	0	0	0	1	1
0	x	x	S <sub>5</sub>	S <sub>6</sub>	0	0	0	1	1	1
x	x	x	S <sub>6</sub>	S <sub>0</sub>	0	0	0	1	1	1

Figure 2: State Transition Table

# STATE ENCODINGS

$$S_0 = 000\ 000$$

$$S_3 = 111\ 000$$

$$S_6 = 000\ 111$$

$$S_1 = 001\ 000$$

$$S_4 = 000\ 001$$

$$S_2 = 011\ 000$$

$$S_5 = 000\ 011$$

## STATE TRANSITION W/ ENCODING

INPUTS			PRESENT STATE						NEXT STATE						OUTPUTS					
reset	l	r	$q_5$	$q_4$	$q_3$	$q_2$	$q_1$	$q_0$	$q_5$	$q_4$	$q_3$	$q_2$	$q_1$	$q_0$	$lc$	$lb$	$la$	$rc$	$rb$	$ra$
1	x	x	x	x	x	x	x	x	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	x	x	0	0	1	0	0	0	0	1	1	0	0	0	0	0	1	0	0	0
0	x	x	0	1	1	0	0	0	1	1	1	0	0	0	0	1	1	0	0	0
x	x	x	1	1	1	0	0	0	0	0	0	0	0	0	1	1	1	0	0	0
0	x	x	0	0	0	0	0	1	0	0	0	0	1	1	0	0	0	0	0	1
0	x	x	0	0	0	0	1	1	0	0	0	1	1	1	0	0	0	0	1	1
x	x	x	0	0	0	1	1	1	0	0	0	0	0	0	0	0	0	1	1	1

Figure 3: State Transition Table with Encodings

## lab\_rm.sv Code

```
module lab3_rm(  
    input logic clk,  
    input logic reset,  
    input logic left, right,  
    output logic lc, lb, la, ra, rb, rc);  
    typedef enum logic [2:0] {S0, S1, S2, S3, S4, S5, S6} statetype;  
    statetype state, nextstate;  
  
    // state register  
    always_ff @(posedge clk, posedge reset)  
    if (reset) state <= S0;  
    else state <= nextstate;  
  
    // next state logic  
    always_comb  
  
    case (state)  
    S0: if (left & ~right & ~reset) nextstate = S1;  
    else if (right & ~left & ~reset) nextstate = S4;  
    else nextstate = S0;  
    S1: if (reset) nextstate = S0;  
    else nextstate = S2;  
    S2: if (reset) nextstate = S0;  
    else nextstate = S3;  
    S3: nextstate = S0;  
    S4: if (reset) nextstate = S0;  
    else nextstate = S5;  
    S5: if (reset) nextstate = S0;  
    else nextstate = S6;  
    S6: nextstate = S0;  
    default: nextstate = S0;  
    endcase  
  
    // output logic  
    assign la = (state==S1 | state==S2 | state==S3);  
    assign lb = (state==S2 | state==S3);  
    assign lc = (state==S3);  
    assign ra = (state==S4 | state==S5 | state==S6);  
    assign rb = (state==S5 | state==S6);  
    assign rc = (state==S6);  
  
endmodule
```

Figure 4: Design SystemVerilog Code

### *testbench\_rm.sv Code*

```
module testbench_rm();
    logic clk, left, right, reset;
    logic lc, lb, la, ra, rb, rc;
    lab3_rm dut(
        clk, reset, left, right,
        lc, lb, la, ra, rb, rc);
    initial
    forever begin
        clk = 0; #50; clk = 1; #50;
    end
    initial begin
        #100;
        left = 1;
        right = 0;
        reset = 0;
        #400;
        left = 0;
        right = 0;
        reset = 1;
        #100;
        left = 0;
        right = 1;
        reset = 0;
        #400;
        left = 0;
        right = 0;
        reset = 1;
        #100;
        left = 1;
        right = 1;
        reset = 0;
        #400;
    end
endmodule
```

*Figure 5: Testbench SystemVerilog Code*

## Simulation Waveforms

 


Figure 6: ModelSim Waveforms

## Discussion

The design uses 10 I/O pins, which corresponds to the clock, reset, left, right, lc, lb, la, ra, rb, rc input/output signals. This matches my expectations because there are 3 lights on each side of the car, amounting to 6 lights total. These outputs are controlled by two inputs left and right. Furthermore, the flip flop is necessary to hold the states in memory along with the requirement for a clock and reset input pin.